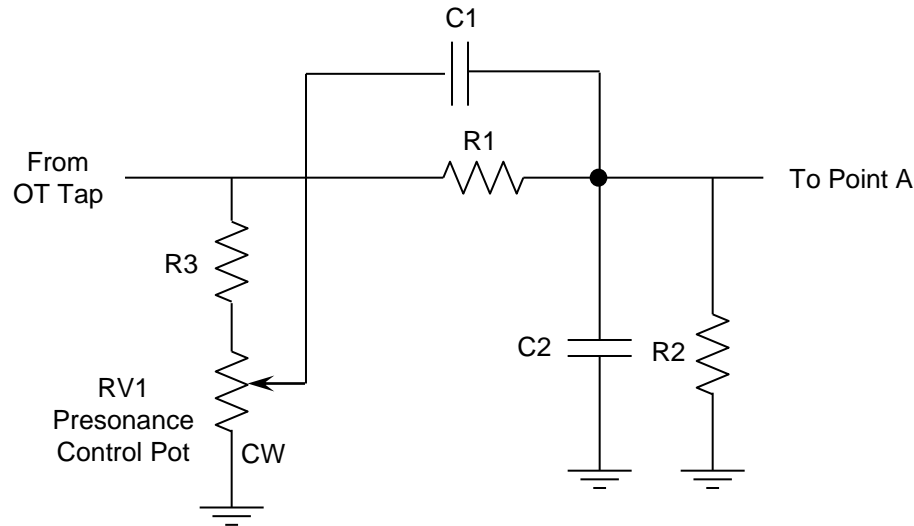


“Presonance” Control for NFB

Martin P Manning January, 2012


Rev. 1, March 2012

Presonance control replaces existing FB and presence NW at right. Choosing component values as described replicates original “Presence” function (CW rotation from 50%) and adds “Resonance” function emphasizing bass (CCW rotation from 50%).



“Presonance” Control

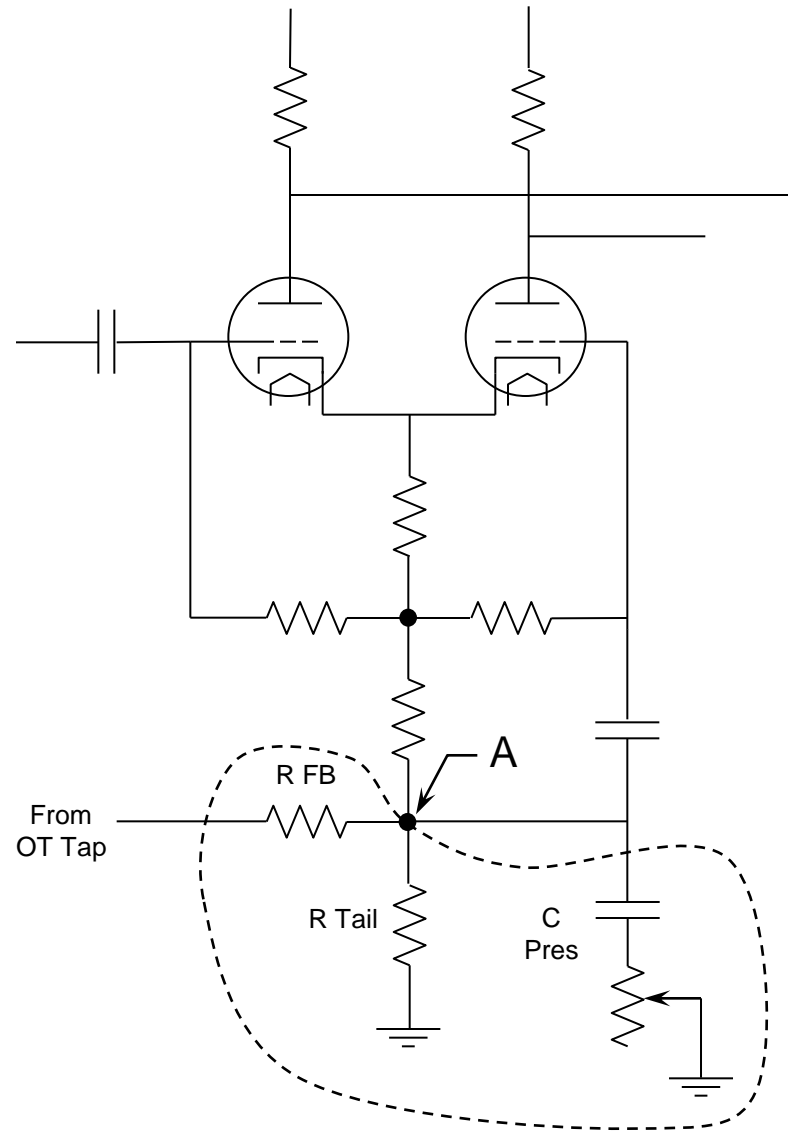$R1 = R_{FB}$
 $R2 = R_{Tail}$
 $R3 = 2 * R_{Tail}$
 $C1 = C_{Pres} * (1 - (R_{FB} / R_{Tail}) / 40)$
 $C2 = C_{Pres} * (R_{FB} / R_{Tail}) / 40$
 (with the intent that $C1 + C2 = C_{Pres}$)
 $RV1 = 2 * R_{Tail}$ to $4 * R_{Tail}$, 10% Audio Taper



Typical Feedback and Presence Control on long-tailed pair phase inverter.

“Presonance” Control for NFB

Martin P Manning January, 2012

Rev. 1, March 2012

Example:

Original circuit $R_{FB} = 100k$, $R_{Tail} = 4k7$, and $C_{Pres} = 0.1\mu F$

